

OPAMP Compensation

Kuntal Kokate *
ee18btech11028@iith.ac.in

1. The op amp in the circuit of Fig. 1.1 has an open-loop gain of 10^5 and a single-pole rolloff with $\omega_{3dB} = 10$ rad/s.

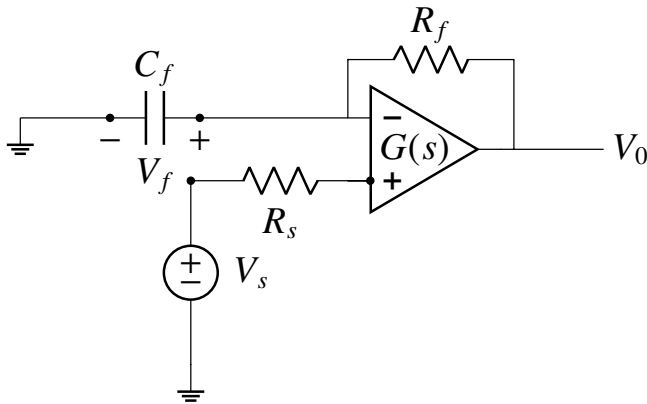


Fig. 1.1

Parameters	Value
C_f	$0.01\mu\text{F}$
R_s	$100k\Omega$
R_f	$100k\Omega$
P_{11}	10 rad/sec

TABLE 1

(a) Sketch a Bode plot for the loop gain. (b) Find the frequency at which $|GH| = 1$, and find the corresponding phase margin. (c) Find the closed-loop transfer function, including its zero and poles. Sketch a pole-zero plot. Sketch the magnitude of the transfer function versus frequency, and label the important parameters on your sketch. (d) Find the unit step response of the system.

2. Sketch a Bode plot for the loop gain.

Solution: Op-amp in our question has an open

loop gain characterised by a single pole P_{11} from table 1 i.e.

$$G(s) = \frac{10^5}{1 + \frac{s}{P_{11}}} \quad (2.1)$$

Using voltage division on Fig. 1.1 we obtain,

$$H(s) = \frac{V_f}{V_o} = \frac{\frac{1}{sC_f}}{R_f + \frac{1}{sC_f}} \quad (2.2)$$

$$\Rightarrow H(s) = \frac{1}{1 + \frac{s}{P_{21}}} \quad (2.3)$$

where,

$$P_{21} = \frac{1}{R_f C_f} = 1000 \quad (2.4)$$

The loop gain is,

$$GH(s) = \frac{10^5}{(1 + \frac{s}{10})(1 + \frac{s}{1000})} \quad (2.5)$$

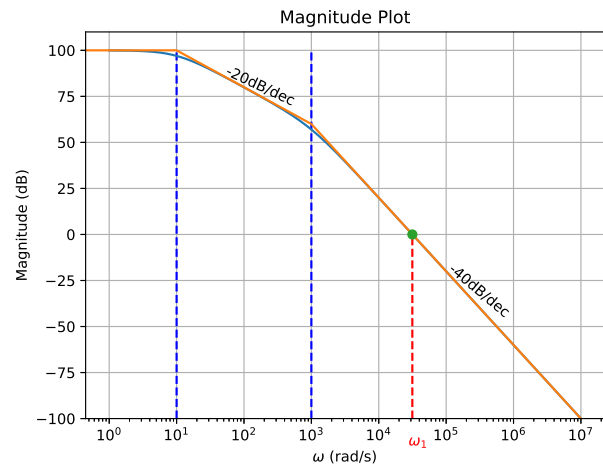


Fig. 2.2: Magnitude plot

3. Find the frequency at which $|GH| = 1$, and find the corresponding phase margin.

Solution: Value of ω for unity magnitude can be obtained from Fig. 2.2 which is approximately 3×10^4 . More precise value can be

*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India. All content in this manual is released under GNU GPL. Free and open source.

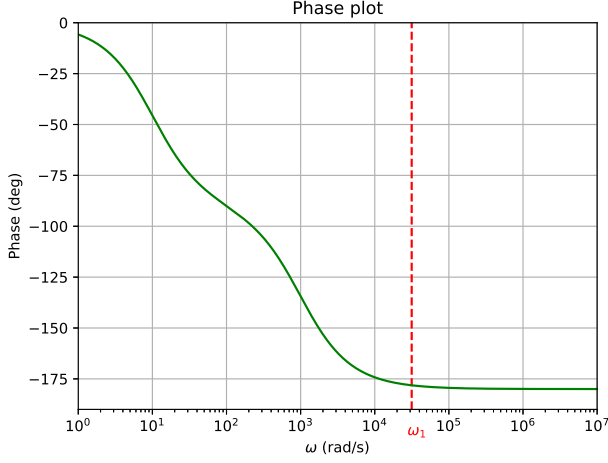


Fig. 2.3: Phase plot

obtained by solving for ω in,

$$\frac{10^5}{\sqrt{1 + \frac{w_1^2}{P_1^2}} \sqrt{1 + \frac{w_1^2}{P_2^2}}} = 1 \quad (3.1)$$

Thus,

$$\omega_1 = 3.15 \times 10^4 \text{ rad/s} \quad (3.2)$$

The phase margin visibly from the Fig. 2.3 is very small.

$$PM = 180^\circ - \tan^{-1}\left(\frac{\omega_1}{10}\right) - \tan^{-1}\left(\frac{\omega_1}{1000}\right) = 1.84^\circ \quad (3.3)$$

4. Find the closed-loop transfer function, including its zero and poles. Sketch a pole-zero plot. Sketch the magnitude of the transfer function versus frequency, and label the important parameters on your sketch.

Solution:

$$T(s) = \frac{G(s)}{1 + G(s)H(s)} \quad (4.1)$$

$$(4.2)$$

From (2.3) and (2.1) we have,

$$\Rightarrow T(s) = \frac{10^6(s + 1000)}{s^2 + 1010s + 10^4 + 10^9} \quad (4.3)$$

$$(4.4)$$

Zeros of closed loop transfer function,

$$Z_1 = -1000 \quad (4.5)$$

Similarly for poles,

$$s^2 + 1010s + 10^4 + 10^9 = 0 \quad (4.6)$$

$$\Rightarrow P_1, P_2 = -505 \pm j31618.9 \quad (4.7)$$

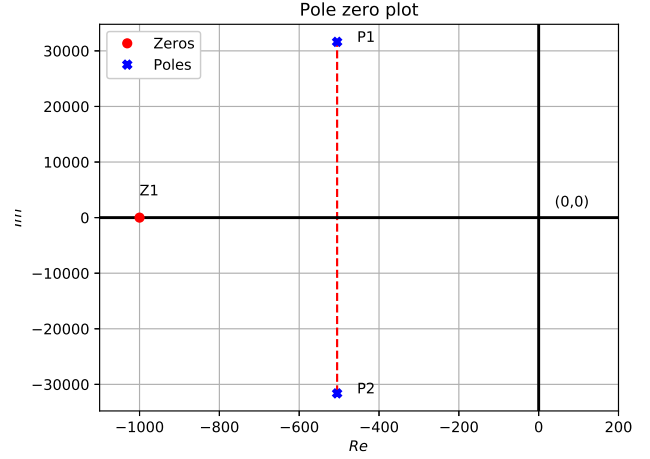


Fig. 4.4: Pole zero plot

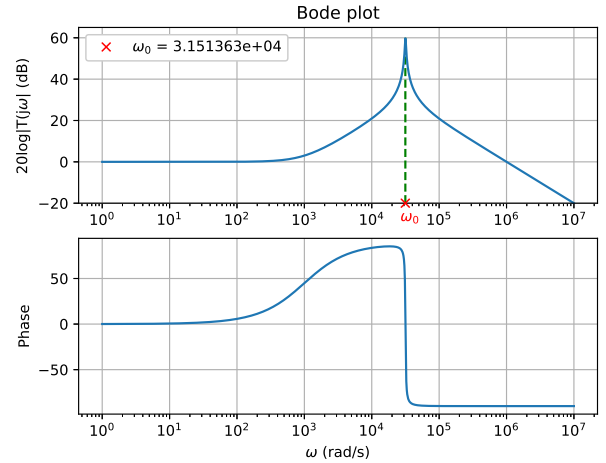


Fig. 4.5: Closed loop bode plot

Poles are at $\omega_0 = 3.16 \times 10^4$

5. Closed loop unit step response.

Solution:

From (4.4) Unit step response is,

$$Y_\gamma(s) = \frac{T(s)}{s} \quad (5.1)$$

We can calculate the steady state output voltage using Final value theorem,

$$\lim_{t \rightarrow \infty} V_o(t) = \lim_{s \rightarrow 0} sY_\gamma(s) \approx 1 \quad (5.2)$$

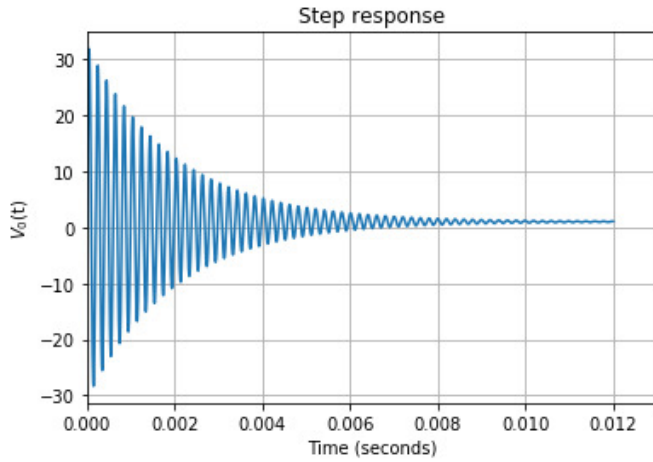


Fig. 5.6: Unit step response

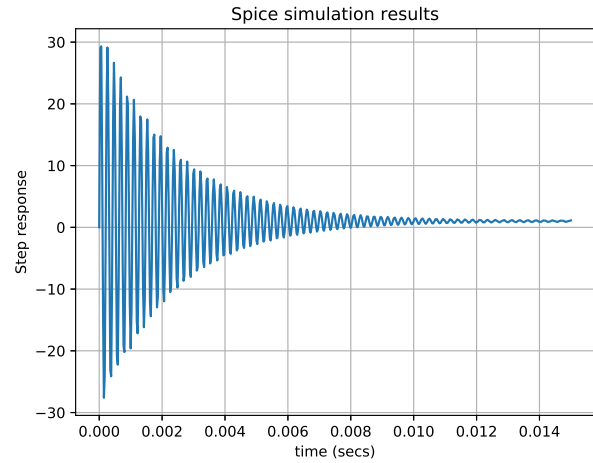


Fig. 6.7: spice simulation step response

which is analogous to plot in fig. 5.6.

6. Simulate the circuit in Ngspice.

Solution: Following readme provides instructions about the simulation

`codes/ee18btech11028/spice/README.md`

The following netlist simulates the closed loop unit step response for circuit in fig. 1.1

`codes/ee18btech11028/spice/step_response.net`

of which data is stored in

`codes/ee18btech11028/spice/ee18btech11028_sim.dat`

which is plotted using python code in,

`codes/ee18btech11028/spice/step.py`

As can be noticed in fig. 6.7 there is very minute difference in amplitude of the initial response of the circuit due to non-ideal nature of the circuit componenets. But rest of the response is identical including the steady state output voltage of 1.

7. Circuit level schematic of op-amp used for simulation, is in fig. 7.8 Since we need a single pole op-amp having $\omega_{3db} = 10\text{rad/s}$ ($f_{p1} = \frac{10}{2\pi}\text{Hz}$), we choose a R_{p1} appropriately and calculate the value of C_{p1} according to our single pole roll off frequency.

$$R_{p1} = 1000\Omega \quad (7.1)$$

$$C_{p1} = \frac{1}{2\pi f_{p1} R_{p1}} \quad (7.2)$$

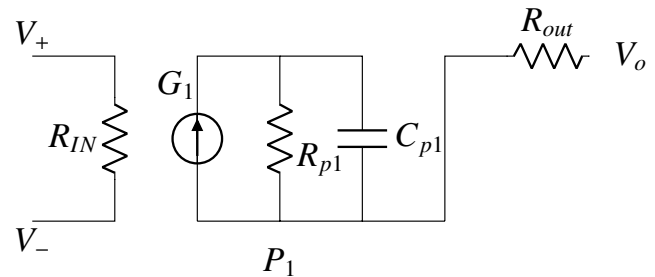


Fig. 7.8

The values corresponding to the components used for op-amp are given in table 7.

Parameters	Value
R_{IN}	$100M\Omega$
R_{p1}	1000Ω
C_{p1}	$100\mu\text{F}$
G_1	$100k$
R_{out}	10Ω

TABLE 7

8. The following python code plots Fig. 2.2, Fig. 2.3, Fig. 4.4, Fig. 4.5 and Fig. 5.6.

`codes/ee18btech11028/ee18btech11028_2.py`